

# CS 210 Homework 5

Alex Vondrak

DUE: Monday, May 7, 2012

Consider the Boolean expression  $e = (x + z)' + (x + y)'z + xy'z$ .

1. Produce the Boolean expression equivalent to  $e$  in canonical sum of minterms form.
2. Give a Karnaugh map for  $e$  and show the minimal set of prime implicants that cover  $e$  and the minimal set of prime implicants that cover  $e'$ .
3. Produce a Boolean expression equivalent to  $e$  in each of the following standard forms:
  - (a) Minimum-literal sum of products
  - (b) Minimum-literal product of sums
  - (c) Minimum-literal inverted sum of products
  - (d) Minimum-literal inverted product of sums
4. Construct a circuit that implements  $e$  using each of the following two-level circuit constructions:
  - (a) NAND-NAND
  - (b) NOR-NOR
  - (c) NAND-AND
  - (d) NOR-OR